

Assignment 1: Using Logical Circuits

Documentation for Calculator


Sean Frommelt

Griffith College





Student ID:	FROSD1602
Course:	1004QBT Foundations of Computing
Tutor:	Shahrzad Saremi
Tutorial:	Thursday, 9:30am – 12:30pm
Due Date:	Friday, 26th August, 2016
Date Submitted:	Friday, 26th August, 2016

Steps to Operate the Calculator

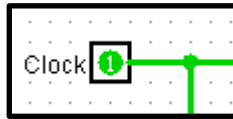
Step 1: Turn the clock to its ON (1) state.



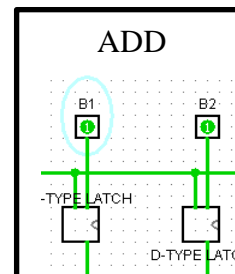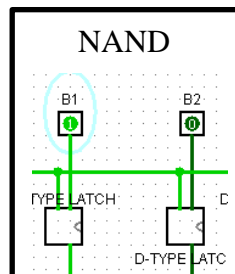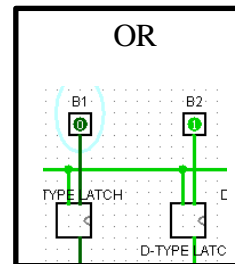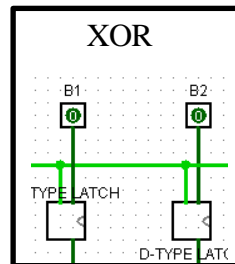
Step 2: To select the one of the four operations, turn the inputs of “B1” and “B2” to one of the corresponding configurations:



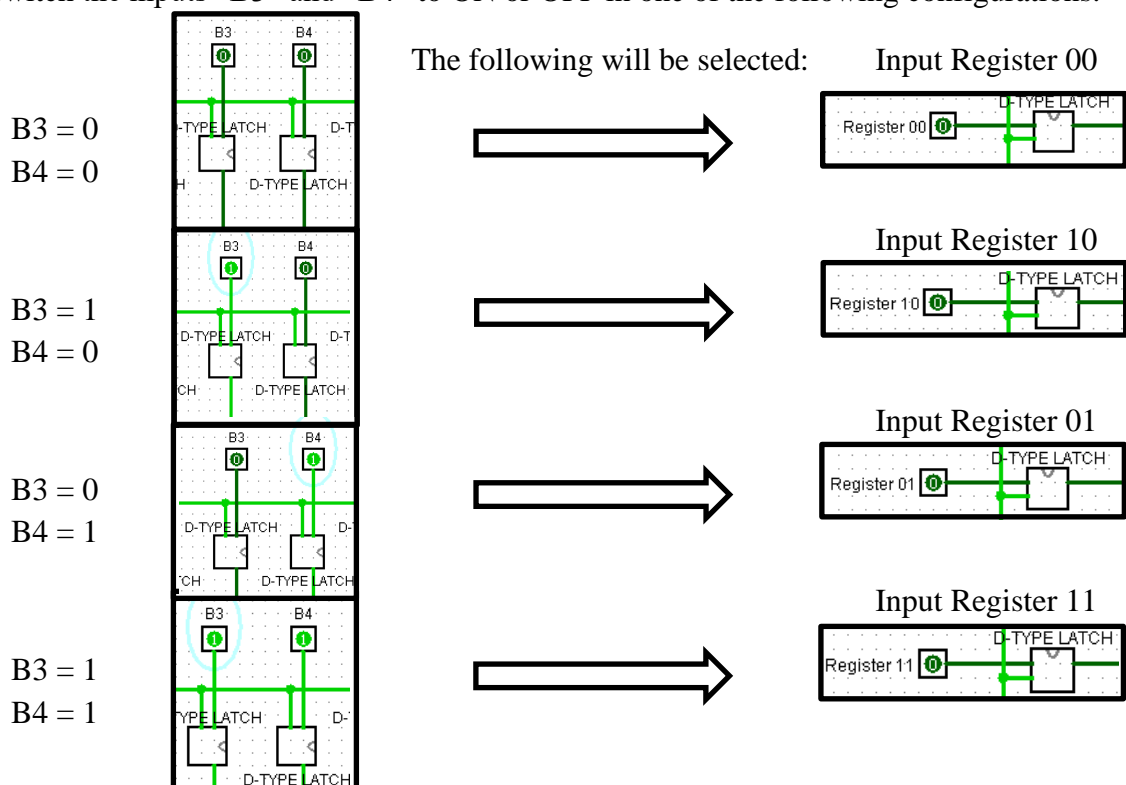Step 3: To select which Input Register will be chosen as the first input to the operation, switch the inputs “B3” and “B4” to ON or OFF in one of the following configurations:



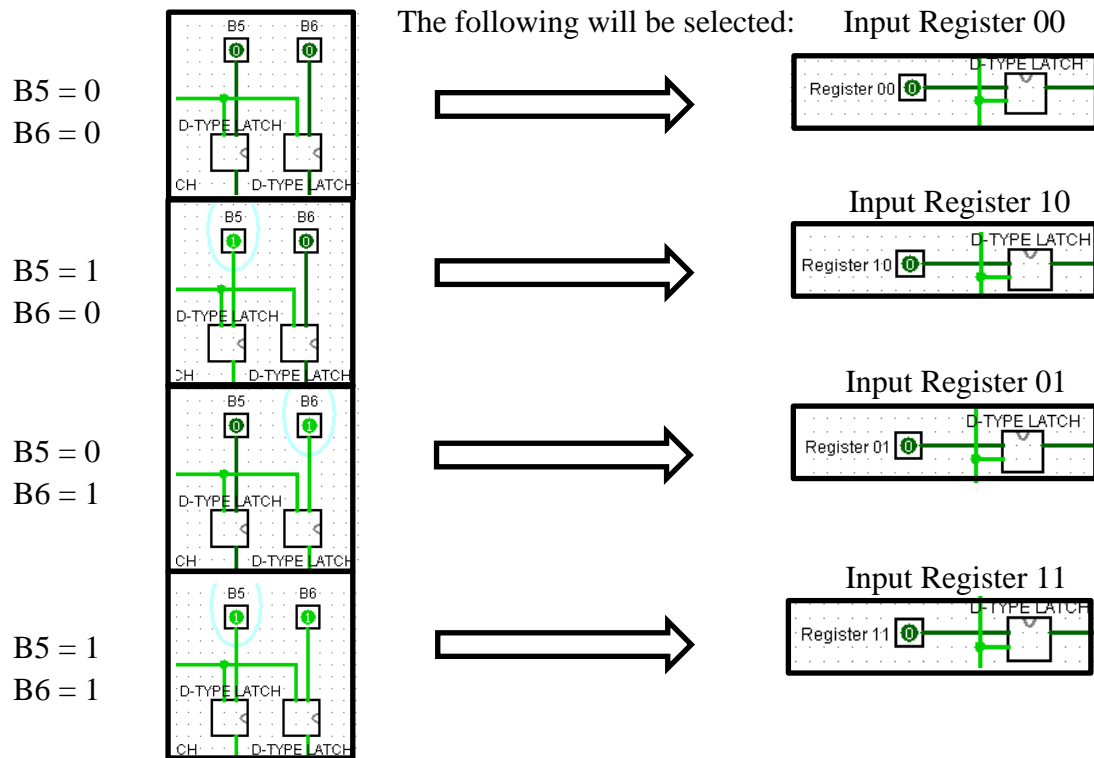Step 4: To select which Input Register will be chosen as the second input to the operation, switch the inputs “B5” and “B6” to ON or OFF in one of the following configurations:




Step 5: Turn the corresponding input registers selected in steps 3 and 4 to the desired ON or OFF state to calculate an output based on the operation you selected in step 2. If the ADD (11) operation was selected in step 2, the carry in can be used in the calculation by switching the “Carry in” input to ON or OFF. The carry out will be displayed by the “Carry out” output.

For example, if the registers selected in steps 3 and 4 were Register 00 and Register 01, and the operation selected in step 2 was the OR (01) operation. Turning Register 00 ON and Register 01 OFF will result in the output displaying an ON state.

Calculator

Below in figure 1 we have the entire two bit binary calculator.


Figure 1

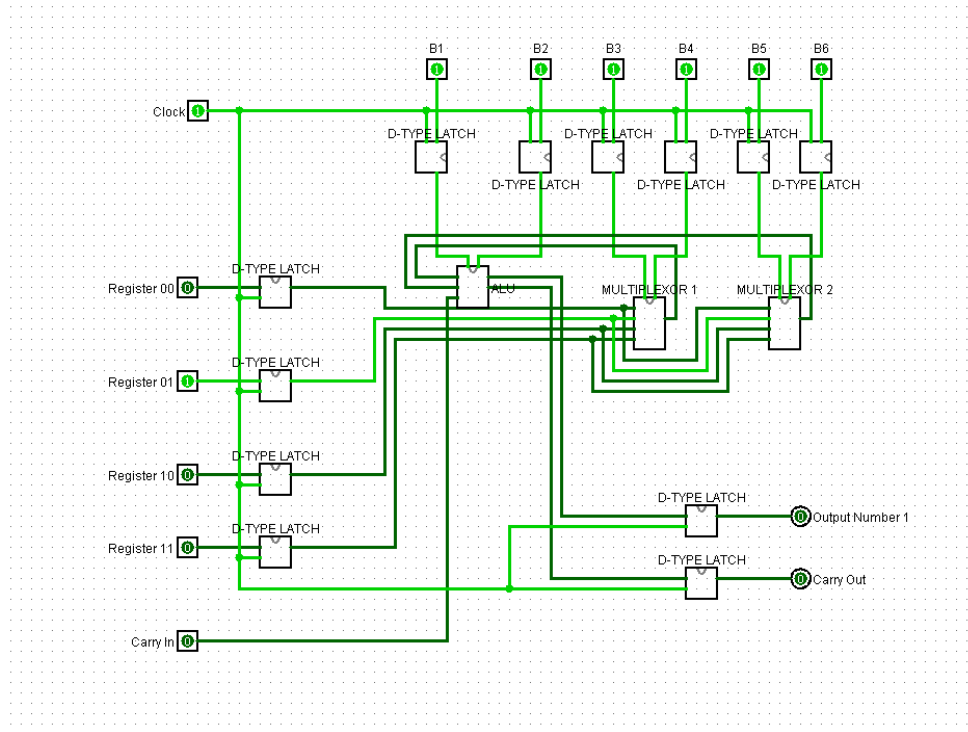


D-Type Latch

The D-Type Latch is shown below in figure 2, it is responsible for storing each input to be used in the calculation.

Figure 2

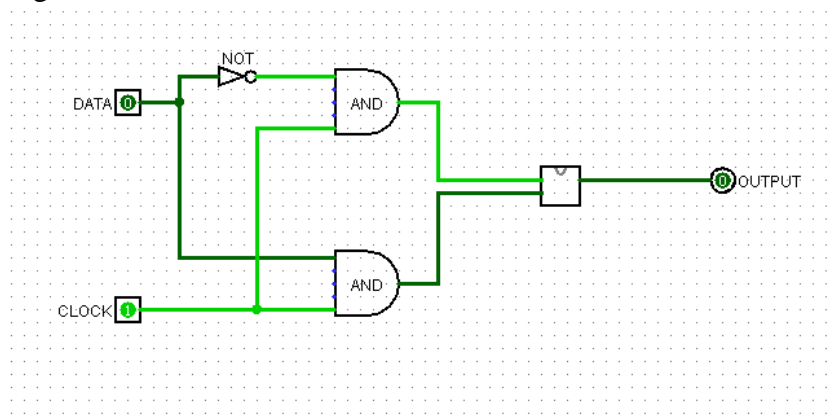


Represented in the Calculator as:

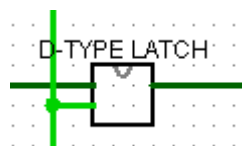


Multiplexor

The Multiplexor is shown below in figure 3, it is responsible for selecting which of the four inputs will be sent to the ALU. The configuration of the opcodes labelled as S1 and S2 will determine which of the four operands labelled as R0, R1, R2 and R3 will be sent to the ALU.

Figure 3

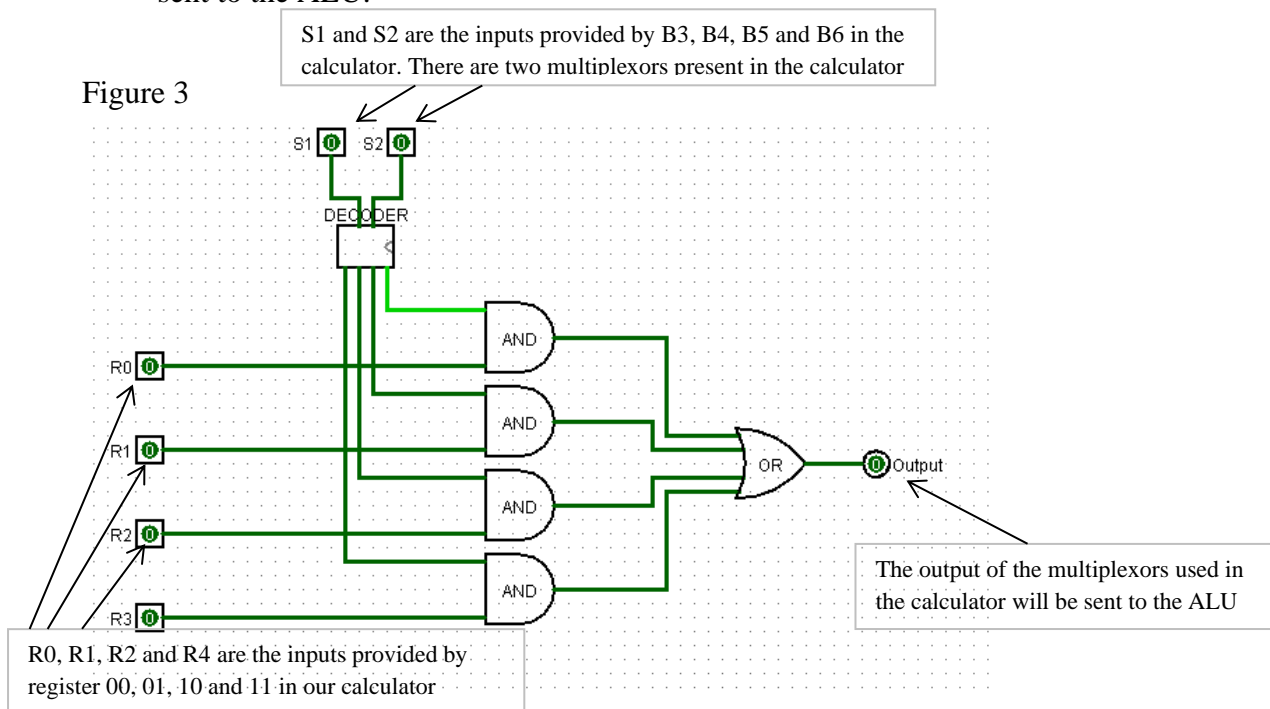


Represented in the Calculator as:

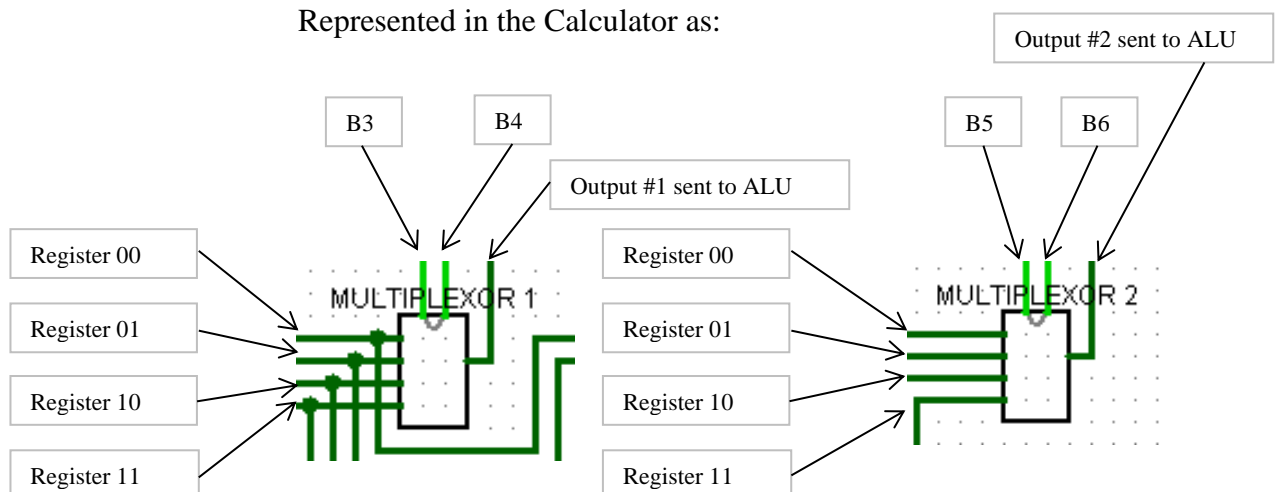

ALU

The ALU is shown below in figure 4, it is responsible for selecting which one of the four operations, XOR, OR, NAND or ADD is applied to the inputs supplied by the multiplexors. We can select one of the four operations: XOR, OR, NAND or ADD by inputting one of the following configurations 00, 01, 10 or 11 with the inputs B1 and B2.

Figure 4

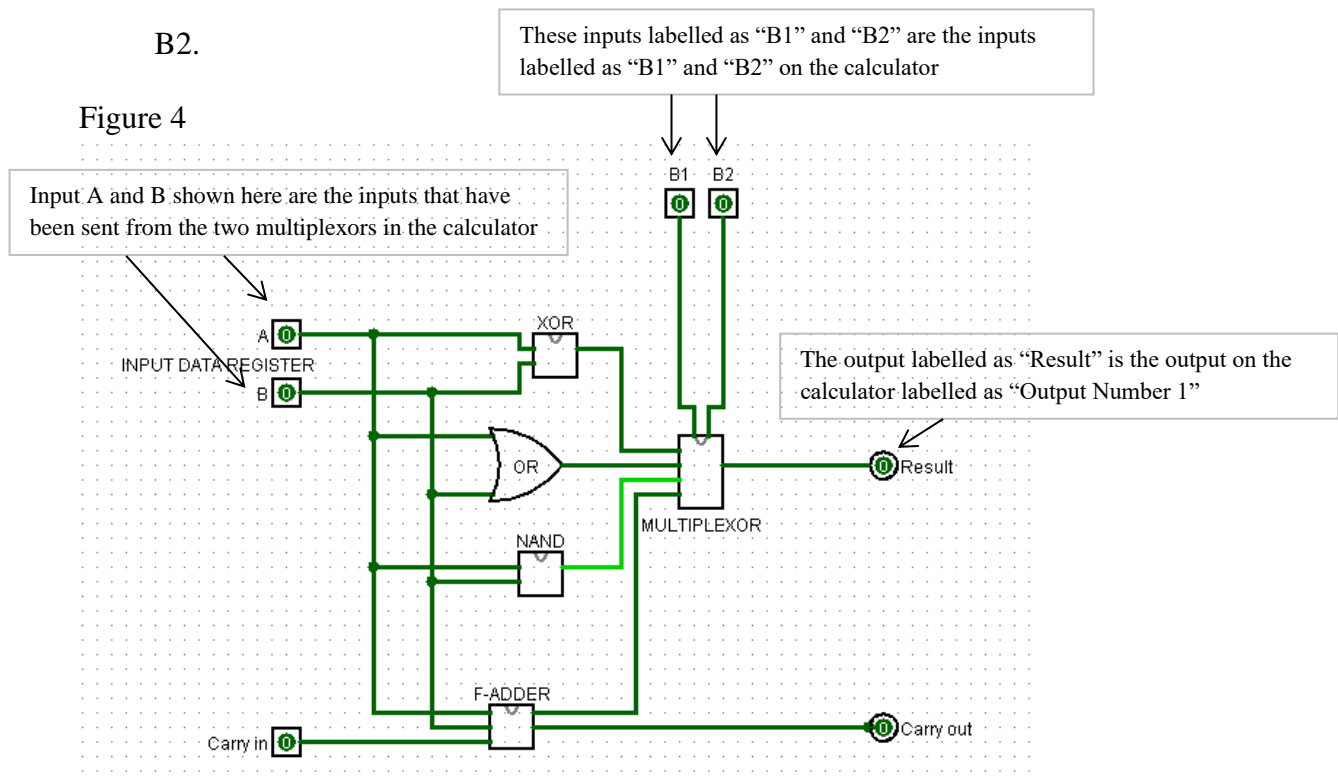

Represented in the Calculator as:

